

ELC251: Electronics I

The College of New Jersey

Department of Electrical and Computer Eng (ECE)

Instructor: Anthony S. Deese, Ph.D.

Quiz and Exam Cheat Sheet

Electrical Basics

$$\mathbf{i}(t) = \frac{dq(t)}{dt} \text{ in Amps}$$

$$\text{Ampere} = \text{Columb/Second}$$

$$\text{Volt} = \frac{kg(m^2)}{As} = A\Omega = \frac{W}{A} = \frac{J}{C}$$

$$W = Ft$$

$$P = \frac{d\mathbf{w}(t)}{dt} = ma = I^2 R = \frac{V^2}{R} \text{ in Watts}$$

$$P = VI$$

remember passive sign convention,
current flows from + to -

$$\text{Ohm's Law: } V = IR$$

Note: passive sign convention states that current flows through a passive element (like a resistor) from positive to negative terminal. This is required for proper implementation of both equations above.

$$\text{Tellegen's Theorem: } \sum_{k=1}^N P_k = 0$$

$$\text{Kirchoff's Current Law (KCL): } \sum_{k=1}^N I_{km} = 0$$

$$\text{Kirchoff's Voltage Law (KVL): } \sum_{k=1}^N V_k = 0$$

$$\text{Impedance: } \vec{Z} = R + jX = \frac{1}{\vec{Y}} = \frac{1}{G + jB}$$

$$V_{ab} = V_a - V_b$$

$$\text{Volt Divider: } V_{Out} = V_{In} \left(\frac{R_2}{R_1 + R_2} \right) \text{ when } R_L \gg R_2$$

$$\text{Current Divider: } I_{out} = I_{In} \left(\frac{R_1}{R_1 + R_2} \right)$$

$$\text{Series R: } R_{eq} = \sum_{k=1}^N R_k$$

$$\text{Series V: } V_{eq} = \sum_{k=1}^N V_k$$

$$\text{Parallel R: } R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$\text{Parallel G: } G_{eq} = \sum_{k=1}^N G_k$$

$$\text{Parallel I: } I_{eq} = \sum_{k=1}^N I_k$$

Note: voltage sources add in series, cannot be combined in parallel. Current sources add in parallel, cannot be combined in series.

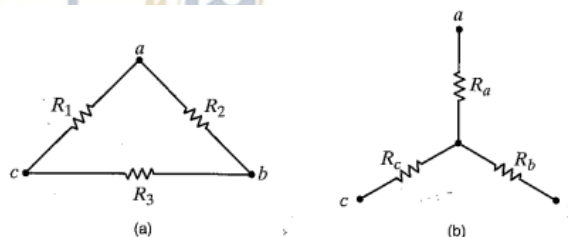


Figure 2.35

Delta and wye resistance networks.

$$R_a = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

$$R_b = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

$$R_c = \frac{R_1 R_3}{R_1 + R_2 + R_3}$$

$$R_1 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_b}$$

$$R_2 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_c}$$

$$R_3 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_a}$$

Nodal Analysis

$$\# \text{ variables/eqns} = N - 1$$

Simple Nodal Analysis By Inspection:
$$\begin{pmatrix} I_{S1} \\ I_{S2} \\ I_{S3} \end{pmatrix} = \underbrace{\begin{pmatrix} +all\ adj\ Ys & -Y_{12} & -Y_{13} \\ -Y_{12} & +all\ adj\ Ys & -Y_{23} \\ -Y_{13} & -Y_{23} & +all\ adj\ Ys \end{pmatrix}}_{\text{admittance matrix}} \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix}$$

to solve:
$$\begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix} = [\underline{Y}]^{-1} \begin{pmatrix} I_{S1} \\ I_{S2} \\ I_{S3} \end{pmatrix}$$

Note: that the basis of nodal analysis is KCL.

Note: that only circuits with independent current sources only can be solved via inspection-based nodal analysis. For others, KCL and KVL must be used.

Note: that symmetry of $[\underline{Y}]$ matrix is lost when circuit contains dependent sources.

Note: that two nodes separated by voltage source may be considered to be supernode.

Table 1: Mesh vs. Nodal Analysis

	nodal	loop/mesh
use?	KCL	KVL
solve for?	voltages	currents
easiest when?	ind current sources only	ind voltage sources only
unit?	nodes (N)	loops (L)
equation?	$I=YV$	$V=ZI$
# unknowns	$N-1$	$B-N+1$

Nodal Analysis

Rules for choosing loops:

- must have $B - N + 1$ branches.
- must include all nodes and branches.

Suggestions for choosing loops:

- any current sources should be isolated and adjacent to only one loop.
- any remaining loops should include no current sources.

Thevenin vs. Norton Equivalent Sources

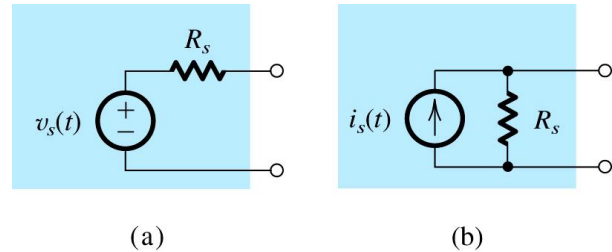


Figure 1: (Left) Thevenin Source and (Right) Norton Source

equiv: $V_s = I_s R_s$ and $R_s = R_s$

Note: that for superposition, independent sources are considered individually. This theorem can only be applied for linear circuits. Sources are removed as follows:

- voltage sources become "shorts"
- current sources become "open ckts"

$$\mathbf{f}(\alpha_1 x_1 + \alpha_2 x_2) = \alpha_1 \mathbf{f}(x_1) + \alpha_2 \mathbf{f}(x_2)$$

How can one find Thevenin Equivalent for a linear circuit? Use two of following four steps:

- Calculate open-ckt term voltage ($V_{OC} = V_{TH}$).
- Calculate short-ckt term current ($I_{SC} = I_{NO}$).
- Calculate equivalent resistance by removing all independent sources ($R_{eq} = R_{Th}$).
- Apply external source and calculate output current.

Note: that you may need nodal / mesh analysis to solve Thevenin / Norton problems.

Note: that inductors act like resistors when it comes to series and parallel connections. For capacitors, this behavior is reversed.

Complex Numbers

$$\begin{aligned} (a + jb) + (c + jd) &= (a + c) + j(b + d) \\ |A|\exp(j\theta) \times |B|\exp(j\theta_B) &= |AB|\exp(j(\theta + \theta_B)) \\ |A|\exp(j\theta) &= \underbrace{|A|\cos(\theta)}_{\text{real}} + j \underbrace{|A|\sin(\theta)}_{\text{imag}} \\ a + jb &= \underbrace{\sqrt{a^2 + b^2}}_{\text{magnitude}} \exp\left(j \underbrace{\tan^{-1}\left(\frac{b}{a}\right)}_{\text{angle in rads}}\right) \end{aligned}$$

Introduction to Electronics

Fourier Series Representation of $f(x)$

$$f(x) = \frac{a_0}{2} + \sum_{k=1}^{\infty} [a_k \cos(kx) + b_k \sin(kx)]$$

$$a_k = \frac{1}{\pi} \int_{-\pi}^{\pi} f(x) \cos(kx) dx, n \geq 0$$

$$b_k = \frac{1}{\pi} \int_{-\pi}^{\pi} f(x) \sin(kx) dx, n \geq 1$$

- $A_0 = \infty \rightarrow (v_{In+} - v_{In-}) = 0$
- $R_{In} = \infty \rightarrow i_{In} = 0$
- $R_{Out} = 0 \rightarrow v_{Out} = A_0 v_{In}$
- $V_{CC+} = \infty, V_{CC-} = -\infty$

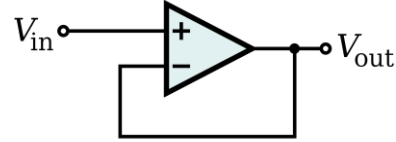


Figure 3: Voltage Follower / Buffer Configuration ($V_{out} = V_{in}$)

	One Filter	The Other
Transfer Function $T(s)$	$\frac{K}{1+(s/\omega_0)}$	$\frac{Ks}{s+\omega_0}$
Magnitude Response $ T(s) $	$\frac{ K }{\sqrt{1+(\omega/\omega_0)^2}}$	$\frac{ K }{\sqrt{1+(\omega_0/\omega)^2}}$
Phase Response $ T(s) $	$-\tan^{-1}(\omega/\omega_0)$	$\tan^{-1}(\omega_0/\omega)$
Transmission at $\omega = 0$	K	0
Transmission at $\omega = \infty$	0	K

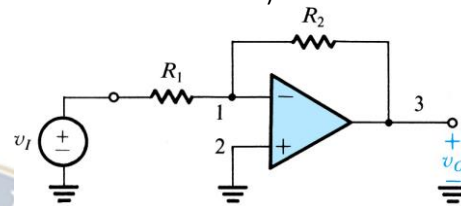


Figure 4: Inverting Op Amp

ideal inverting: $v_O = \left(\frac{-R_2}{R_1}\right) v_I$

for $A \ll \infty$: $v_O = \left(\frac{-R_2/R_1}{1 + \left(\frac{1 + R_2/R_1}{A}\right)}\right) v_I$

freq dependent: $v_O = \left(\frac{-R_2/R_1}{1 + s\left(\frac{1 + R_2/R_1}{\omega_t}\right)}\right) v_I$

Introduction to Operational Amplifiers

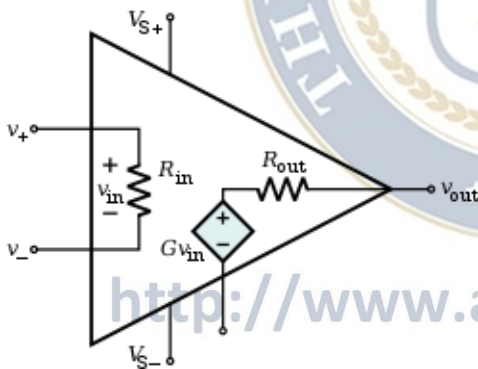


Figure 2: Operational Amplifier Where $G = A_0$ and

$$V_{CC+} = V_{S+}$$

ideal: $v_{Out} = A_0(v_{In+} - v_{In-})$
if $R_{Out}=0, R_{In}=\infty$

actual: $v_{Out} = A_0 \underbrace{(v_{In+} - v_{In-})}_{v_{In}} - i_{Out} R_{Out}$

Note: that output of amplifier cannot exceed supplied voltages $V_{CC+} = V_{S+}$ and $V_{CC-} = V_{S-}$.

Ideal Op-Amp Characteristics:

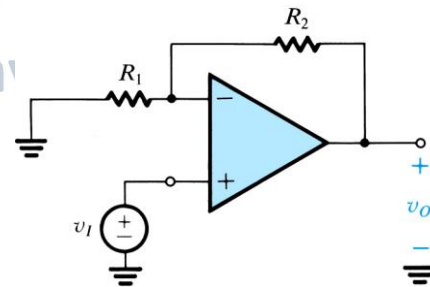


Figure 5: Non-Inverting Amplifier Configuration

ideal non inverting: $v_O = \left(1 + \frac{R_2}{R_1}\right) v_I$

for $A \ll \infty$: $v_O = \left(\frac{1 + R_2/R_1}{1 + \left(\frac{1 + R_2/R_1}{A}\right)}\right) v_I$

freq dependent: $v_o = \left(\frac{1 + R_2/R_1}{1 + s \left(\frac{1 + R_2/R_1}{\omega_t} \right)} \right) v_i$


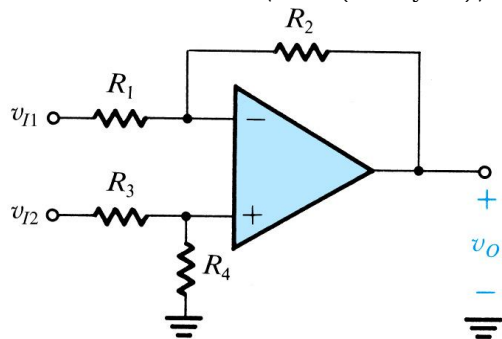


Figure 6: Difference Amplifier Configuration

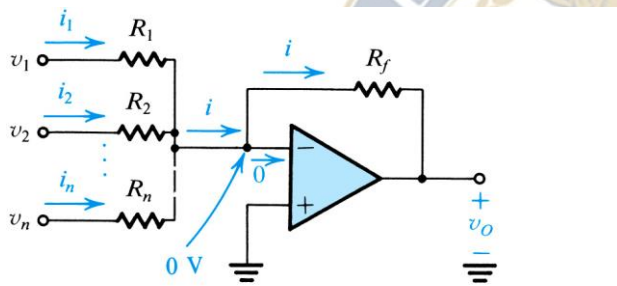ideal difference: $v_o = \frac{(R_1 + R_2)R_4}{(R_3 + R_4)R_1} v_{I2} - \frac{R_2}{R_1} v_{I1}$
 $= \frac{R_2}{R_1} (v_{I2} - v_{I1})$ if $\begin{pmatrix} R_1 = R_3 \\ R_2 = R_4 \end{pmatrix}$



$v_o = - \left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \dots + \frac{R_f}{R_n} v_n \right)$

Figure 7: Summing Amplifier Configuration

Differential vs. Common-Mode

$v_o = A_D v_{DIn} + A_{CM} v_{CMIn}$
 $v_{CMIn} = \frac{1}{2} (v_{In1} + v_{In2})$ and $v_{In1,2} = v_{CMIn} \pm \frac{v_{DIn}}{2}$
 $CMRR = 20 \log_{10} \left(\frac{A_D}{A_{CM}} \right)$

Integrators and Differentiating Op-Amps

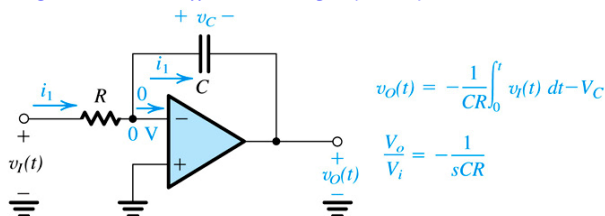


Figure 8: Integrating Amplifier Configuration without Feedback Resistance

$\tau = RC$ and $\omega_0 = \frac{1}{RC}$

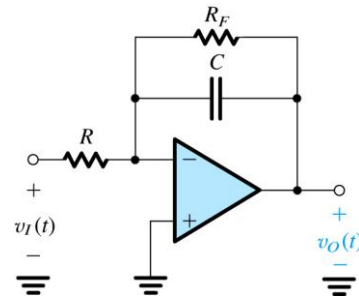


Figure 9: Integrating Amplifier with Feedback Resistance

steady state: $\frac{v_o}{v_i} = -\frac{R_F/R_1}{1 + sR_FC_F}$

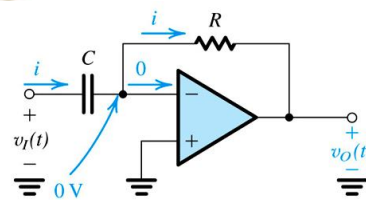


Figure 10: Differentiator Amplifier Configuration

transient: $v_o(t) = -R_F C_1 \frac{dv_i(t)}{dt}$

steady state: $\frac{V_o(s)}{V_i(s)} = -sR_FC_1$

Offset Voltage

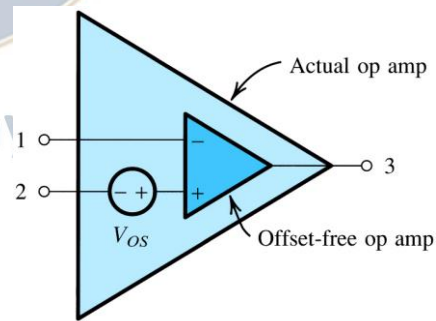


Figure 11: Example of Offset Voltage

$v_o = V_{OS} \left(1 + \frac{R_F}{R_1} \right)$

slope for 1st order low pass behavior
= -20dB/decade

decades btw frequencies: $n_{DEC} = \log\left(\frac{f_2}{f_1}\right)$

$$f_2 = f_1(10^{n_{DEC}})$$

Introduction to Semiconductor Physics

$$n_i = BT^{3/2} \exp(-E_g/2kT)$$

$$B = 7.3 \times 10^{15} \text{ cm}^{-3} \text{ K}^{-3/2}$$

$$E_g = 1.12 \text{ eV for silicon}$$

$$k = 8.62 \times 10^{-5} \frac{\text{eV}}{\text{K}} = 1.38 \times 10^{-23} \text{ J/K}$$

$$q = 1.6 \times 10^{-19} \text{ C}$$

$$p_p \times n_p = n_i^2 \text{ and } p_n \times n_n = n_i^2$$

$$\mu_p = \frac{480 \text{ cm}^2}{\text{Vs}} \text{ for silicon}$$

$$\mu_n = \frac{1350 \text{ cm}^2}{\text{Vs}} \text{ for silicon}$$

$$v_{p\text{-drift}} = \mu_p E \text{ and } v_{n\text{-drift}} = -\mu_n E$$

$$I_p = Aq p v_{p\text{-drift}} \text{ and } I_n = -Aq n v_{n\text{-drift}}$$

$$I = I_p + I_n$$

$$J = I/A$$

$$\sigma = \frac{1}{\rho} = q(p\mu_p + n\mu_n)$$

$$J_p = -qD_p \frac{dp(x)}{dx} \text{ and } J_n = -qD_n \frac{dn(x)}{dx}$$

$$D_p = \frac{12 \text{ cm}^2}{\text{s}} \text{ and } D_n = \frac{35 \text{ cm}^2}{\text{s}} \text{ for silicon}$$

$$J_{tot} = J_p + J_n$$

$$\frac{D_n}{\mu_n} = \frac{D_p}{\mu_p} = V_T \approx 25.8 \text{ mV}$$

$$V_0 = V_T \ln\left(\frac{N_A N_D}{n_i^2}\right)$$

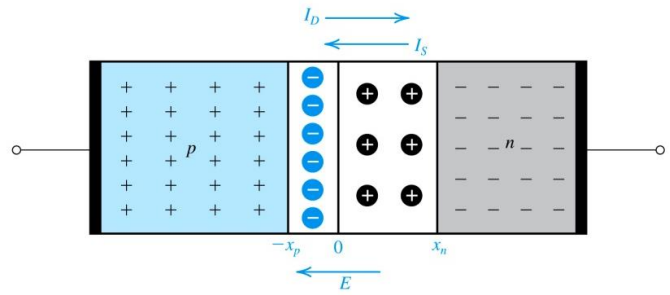


Figure 12: pn-Junction Example

$$Q_J = |Q_{\pm}| = Aq \left(\frac{N_A N_D}{N_A + N_D} \right) W$$

$$Q_J = |Q_{\pm}| = A \sqrt{2\epsilon_s q \left(\frac{N_A N_D}{N_A + N_D} \right) (V_0 - V_F)} \text{ or } V_0 + V_R$$

$$\epsilon_s = 11.7\epsilon_0 = 1.04 \times 10^{-12} \text{ F/cm}$$

$$W = \sqrt{\frac{2\epsilon_s}{q} \left(\frac{1}{N_A} + \frac{1}{N_D} \right) (V_0 - V_F)} \text{ or } V_0 + V_R$$

$$i_D = I_S \left(\exp\left(\frac{v_D}{V_T}\right) - 1 \right) \approx I_S \exp\left(\frac{v_D}{V_T}\right) \text{ if } v_D \gg V_T$$

$$I_S = Aq n_i^2 \left(\frac{D_p}{L_p N_D} + \frac{D_n}{L_n N_A} \right)$$

Diode Basics

$$i_D = I_S (e^{v_D/V_T} - 1) \approx I_S (e^{v_D/V_T})$$

$$V_T = \frac{kT}{q} = 25.8 \text{ mV (unless stated otherwise)}$$

$$v_D = V_T \ln\left(\frac{i_D}{I_S}\right)$$

$$\frac{\Delta V_D}{\Delta T} = \frac{-2 \text{ mV}}{1^\circ \text{C}} \text{ approximately}$$

Iterative Analysis for Diode

Step #1: Start with initial guess of $v_D^{(0)}$.

Step #2: Use nodal or mesh analysis to solve for $i_D^{(0)}$.

Step #3: Use exponential model to update $v_D^{(1)}$.

Step #4: Repeat Steps #1 through #3 until convergence.

Small-Signal Model for Diode

$$i_D = I_D + i_d$$

steady state: $I_D = I_S \exp(V_D/V_T)$
 $V_D = 700\text{mV}$

total instantaneous: $i_D = \left[I_S \exp\left(\frac{V_D}{V_T}\right) \right] \exp\left(\frac{v_d}{V_T}\right)$
 I_D

total instantaneous: $i_D \approx I_D + \left(\frac{I_D}{V_T}\right) v_d$
small signal approximation

$$r_d = \frac{V_T}{I_D}$$

$v_d < 5\text{mV}_{amp}$ for small signal approximation

Full-Wave Rectifier with Filter Capacitor



$$V_r(\text{peak to peak}) \approx V_{peak} \left(\frac{T}{RC} \right)$$

$$\Delta t = \frac{\sqrt{2V_r/V_{peak}}}{\omega}$$

Linearization

$$f(x) \approx \left(\left[\frac{df}{dx} \right]_{x=x_0} \right) (x - x_0) + f(x_0)$$

MOSFET-Basics

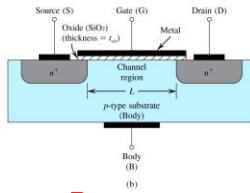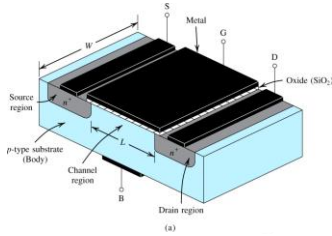

$$\epsilon_0 = 3.45 \times 10^{-11} \text{ in } \frac{\text{F}}{\text{m}}$$

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} \text{ in } \frac{\text{F}}{\text{m}^2}$$

$$v_{OV} = v_{GS} - V_t \text{ in } V$$

$$v_{GD} = v_{GS} - v_{DS} = V_t + v_{OV} - v_{DS} \text{ in } V$$

$$k_n = \frac{C_{ox} \mu_n}{k'_n} \left(\frac{W}{L} \right) \text{ in } \frac{A}{V^2}$$

Charge Stored in P/N-Channel

$$v_{DS} < 50\text{mV}: |Q| = C_{ox}(WL)v_{OV} \text{ (rectangle)}$$

$$\text{triode: } |Q| = C_{ox}(WL) \left(v_{OV} - \frac{1}{2} v_{DS} \right) \text{ (trapezoid)}$$

$$\text{saturation } v_{GS} > V_t: |Q| = \frac{1}{2} C_{ox}(WL)v_{OV} \text{ (tri)}$$



i_D vs. v_{DS} Relationship

$$v_{DS} < 50\text{mV}: i_D = (k_n v_{OV}) v_{DS} \text{ in } A$$

$$v_{DS} < 50\text{mV}: r_{DS} = \frac{v_{DS}}{i_D} = \frac{1}{k_n v_{OV}} \text{ in } \Omega$$

$$\text{triode: } i_D = k_n \left(v_{OV} - \frac{1}{2} v_{DS} \right) v_{DS}$$
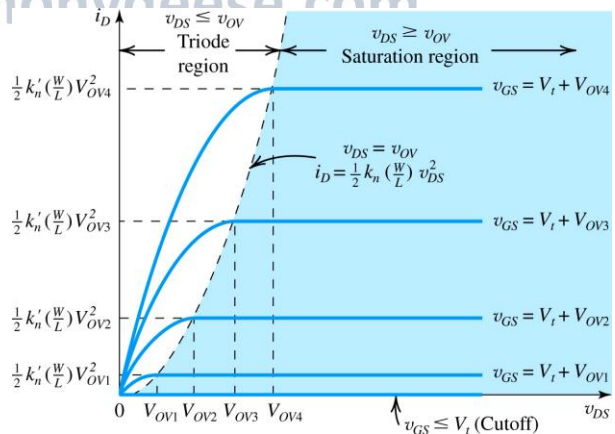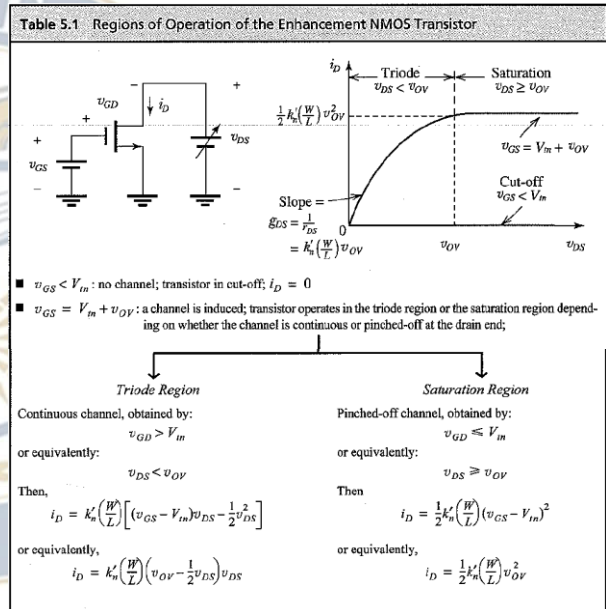
$$\text{saturation } v_{GS} > V_t: i_D = \frac{1}{2} k_n v_{OV}^2$$



Channel Length Modulation

saturation $v_{GS} > V_t$: $i_D = \frac{1}{2} k_n v_{OV}^2 (1 + \lambda)$

output resistance: $r_D = \left(\frac{1}{2} k_n v_{OV}^2 \lambda \right)^{-1} = \frac{V_A}{i_D}$

MOSFET-Based Amplifier

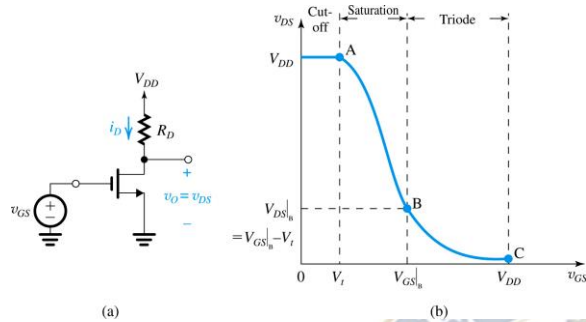


Figure 14: MOSFET Amplifier Configuration

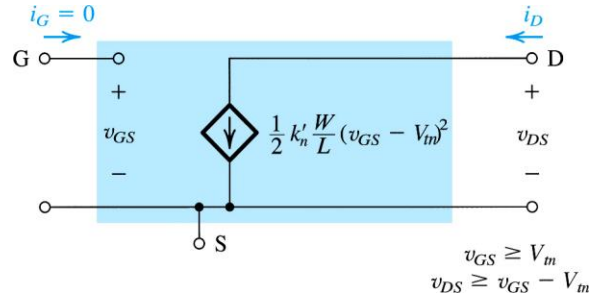


Figure 15: MOSFET Equivalent Circuit in Saturation Region

$v_{DS} = V_{DD} - i_D R_D$ in V

$v_{DS} = V_{DD} - \left(\frac{1}{2} k_n v_{OV}^2 \right) R_D$ in V
assuming saturation

$V_{GS|A} = V_t$ in V

$V_{GS|B} = V_t + \frac{\sqrt{2k_n R_D V_{DD} + 1} - 1}{k_n R_D}$ in V

$A_v = -k_n V_{OV} R_D$
use static/DC component of v_{OV}

amplifies TV only: $v_{ds} = A_v v_{gs}$

$\max(A_v) = -10V_{DD}$

SI Units

TABLE 1.5 Selected Prefixes Used in the Metric System

Prefix	Abbreviation	Meaning	Example
Giga	G	10^9	1 gigameter (Gm) = 1×10^9 m
Mega	M	10^6	1 megameter (Mm) = 1×10^6 m
Kilo	k	10^3	1 kilometer (km) = 1×10^3 m
Deci	d	10^{-1}	1 decimeter (dm) = 0.1 m
Centi	c	10^{-2}	1 centimeter (cm) = 0.01 m
Milli	m	10^{-3}	1 millimeter (mm) = 0.001 m
Micro	μ^a	10^{-6}	1 micrometer (μ m) = 1×10^{-6} m
Nano	n	10^{-9}	1 nanometer (nm) = 1×10^{-9} m
Pico	p	10^{-12}	1 picometer (pm) = 1×10^{-12} m
Femto	f	10^{-15}	1 femtometer (fm) = 1×10^{-15} m

^aThis is the Greek letter mu (pronounced "mew").

temperature converion: $\text{Kelvin} = 273^0 + \text{Celsius} = \frac{5}{9} (\text{Fahrenheit} + 459.67)$